

**Second Semester B.E./B.Tech. Degree Examination, June/July 2024**  
**Introduction to Electronics and Communication**

Time: 3 hrs.

Max. Marks: 100

*Note: 1. Answer any FIVE full questions, choosing ONE full question from each module.  
 2. M : Marks , L: Bloom's level , C: Course outcomes.*

Module – 1			M	L	C
Q.1	a.	Draw the block diagram of Regulated power supply and mention the function of each block.	8	L2	CO1
	b.	With the use of circuit diagram and waveforms, explain the working of Half wave rectifier with capacitor filter.	8	L2	CO1
	c.	Mention advantages of –ve feedback.	4	L1	CO1
<b>OR</b>					
Q.2	a.	List out and explain the various types of amplifiers.	8	L1	CO1
	b.	With neat diagram, explain the concept of negative feedback amplifier.	7	L2	CO1
	c.	Write a note on Multistage amplifiers.	5	L1	CO1
<b>Module – 2</b>					
Q.3	a.	Explain the working of RC – ladder network oscillator.	6	L2	CO2
	b.	Define Multivibrators. Explain the working of single stage astable multivibrator with diagram.	8	L1	CO2
	c.	Explain its working of Weinbridge Oscillator with diagram.	6	L2	CO2
<b>OR</b>					
Q.4	a.	Define the following terms with respect to the Op_Amp : i) CMRR ii) Slew rate    iii) Supply voltage rejection ratio iv) Input offset voltage    v) Input offset current.	10	L1	CO2
	b.	Explain how Op_Amp can be used as i) Voltage follower    ii) Integrator.	10	L2	CO2
<b>Module – 3</b>					
Q.5	a.	Convert i) $(3568)_{10} = (?)_2$ ii) $(3FD)_{16} = (?)_2$ iii) $(110111)_2 = (?)_{10}$ iv) $(1234)_{10} = (?)_8$ v) $(5678)_{10} = (?)_{16}$ .	10	L2	CO3
	b.	Write any four Boolean theorems and Identities.	10	L1	CO3
<b>OR</b>					
Q.6	a.	Simplify the following Boolean functions : i) $Y = A\bar{B} + AB$ ii) $F = B[(A + \bar{B})(B + C)]$ iii) $Z = B(A + C) + C$ .	8	L3	CO3

	b.	Explain Half adder circuit with truth table, Realize the circuit for sum and carry using basic gates.	8	L2	CO3
	c.	Write the Symbol and Truth Table of AND and OR – Gate.	4	L1	CO3
<b>Module – 4</b>					
Q.7	a.	Define Embedded system and explain the classification of Embedded system based on Complexity and Deterministic behavior.	10	L2	CO4
	b.	Compare Embedded system and General computing system.	6	L1	CO4
	c.	List out the major applications areas of Embedded system.	4	L1	CO4
<b>OR</b>					
Q.8	a.	With the use of diagram, explain the core of an Embedded system.	8	L2	CO4
	b.	Compare RISC and CISC.	6	L1	CO4
	c.	Write a short notes on Sensors and 7 – segment LED displays.	6	L2	CO4
<b>Module – 5</b>					
Q.9	a.	With the help of block diagram, explain the basic Communication system.	10	L2	CO5
	b.	Define Noise and explain the various kinds of noises.	10	L2	CO5
<b>OR</b>					
Q.10	a.	Define Multiplexing and explain types of Communication systems.	8	L2	CO5
	b.	Classify and explain the Multiple Access Techniques.	8	L2	CO5
	c.	Mention the Need for Modulation.	4	L1	CO5

\*\*\*\*\*