

131

**Vivekananda College of Engineering & Technology, Puttur**  
 [A Unit of Vivekananda Vidyavardhaka Sangha Puttur ®]  
 Affiliated to VTU, Belagavi & Approved by AICTE New Delhi

CRM08

Rev 1.15 (2024 rev)

<CS>

<14.10.2024>

**CONTINUOUS INTERNAL EVALUATION - 1**

Dept: AI/ CD/ CS	Sem / Div: 3 AI/ CD/ CS A & B	Sub: Digital Design and Computer Organization	S Code: BCS302
Date: 18.10.2024	Time: 2:30-4:00	Max Marks: 50	Elective: N

Note: Answer any 2 full questions, choosing one full question from each part.

QN	Questions	Marks	RBT	CO's
<b>PART A</b>				
1 a	Identify the prime implicants and essential prime implicants of the following functions: (i) $F(A, B, C, D) = \sum m(1, 3, 4, 5, 10, 11, 12, 13, 14, 15)$ (ii) $F(W, X, Y, Z) = \sum m(0, 1, 2, 5, 7, 8, 10, 15)$	10	L3	CO1
b	With neat diagram, explain the basic operational concepts between processor and memory	9	L2	CO3
c	Simplify and implement the following Boolean function using NAND Gates: $F(x, y, z) = \sum m(1, 2, 3, 4, 5, 7)$	6	L3	CO1
<b>OR</b>				
2 a	Determine the minimum SOP form from using Karnaugh Map and draw the circuit diagram: (i) $F = A'B'C' + B'CD' + A'BCD' + AB'C'$ (ii) $F = x'z' + wyz + w'y'z' + x'y + wxy'z' + w'xyz$	10	L3	CO1
b	Explain the following: (i) Processor time & Processor cache (ii) Basic performance equation (iii) Performance measurement	9	L2	CO3

c Using gate-level description & continuous assignment statements (data flow description), write a Verilog description of the circuit shown in the following Figure:

 


Figure Q2c

$$F = A(CD + B) + BC'$$

6

L3

CO1

### PART B

3 a Implement the design of combinational circuit – BCD to Excess-3 Code Converter

10

L2

CO2

b Realize the following Boolean functions using 8:1 MUX with  $A, B, C$  as Select lines and 4:1 MUX with  $A, B$  as Select lines:  $Y(A, B, C, D) = \sum m(0, 1, 5, 6, 7, 11, 15)$

9

L3


CO2

c Write Verilog descriptions for D flip-flop and JK flip-flop

6

L3

CO2

 

### OR

4 a Design and explain four-bit adder

10

L2

CO2

b Define decoder. Describe the working principle of a 3:8 decoder. Draw the logic diagram of the 3:8 decoder with enable input. Realize the following Boolean expressions using a 3:8 decoder and multi-input OR gates:

$$F1(A, B, C) = \sum m(1, 3, 7) \quad F2(A, B, C) = \sum m(2, 3, 5)$$

9

L3

CO2

c What is a Latch? With neat diagram, explain SR latch using NOR Gate.

6

L3

CO2